

Timing Considerations with Verilog-Based Designs

This tutorial describes how Altera's Quartus[®] II software deals with the timing issues in designs based on the Verilog hardware description language. It discusses the various timing parameters and explains how specific timing constraints may be set by the user.

Contents:

- Example Circuit
- Timing Analyzer Report
- Specifying the Timing Constraints
- Timing Simulation

Quartus II software includes a Timing Analyzer module which performs a detailed analysis of all timing delays for a circuit that is compiled for implementation in an FPGA chip. This tutorial discusses the types of analyses performed and shows how particular timing requirements may be specified by the user. The discussion assumes that the reader is familiar with the basic operation of Quartus II software, as may be learned from an introductory tutorial.

Doing this tutorial, the reader will learn about:

- Parameters evaluated by the Timing Analyzer
- Specifying the desired values of timing parameters
- Using timing simulation

The timing results shown in the examples in this tutorial were obtained using Quartus II version 5.0, but other versions of the software can also be used.

1 Example Circuit

Timing issues are most important in circuits that involve long paths through combinational logic elements with registers at inputs and outputs of these paths. As an example, we will use the adder/subtractor circuit shown in Figure 1. It can add, subtract, and accumulate n -bit numbers using the 2's complement number representation. The two primary inputs are numbers $A = a_{n-1}a_{n-2} \cdots a_0$ and $B = b_{n-1}b_{n-2} \cdots b_0$, and the primary output is $Z = z_{n-1}z_{n-2} \cdots z_0$. Another input is the *AddSub* control signal which causes $Z = A + B$ to be performed when *AddSub* = 0 and $Z = A - B$ when *AddSub* = 1. A second control input, *Sel*, is used to select the accumulator mode of operation. If *Sel* = 0, the operation $Z = A \pm B$ is performed, but if *Sel* = 1, then B is added to or subtracted from the current value of Z . If the addition or subtraction operations result in arithmetic overflow, an output signal, *Overflow*, is asserted.

To make it easier to deal with asynchronous input signals, they are loaded into flip-flops on a positive edge of the clock. Thus, inputs A and B will be loaded into registers *Areg* and *Breg*, while *Sel* and *AddSub* will be loaded into flip-flops *SelR* and *AddSubR*, respectively. The adder/subtractor circuit places the result into register *Zreg*.

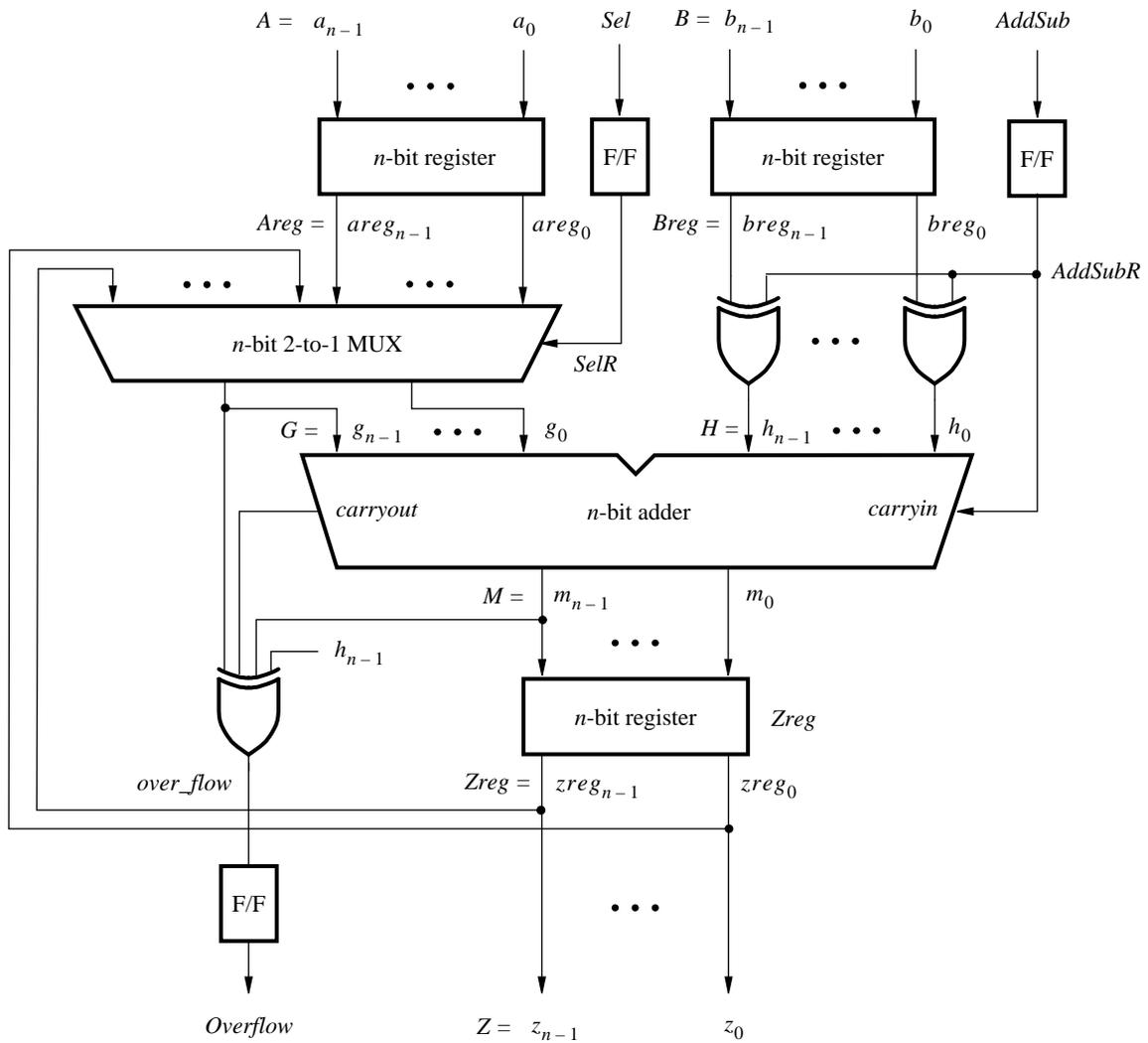


Figure 1. The adder/subtractor circuit.

The required circuit is described by the Verilog code in Figure 2. For our example, we use a 16-bit circuit as specified by $n = 16$. Implement this circuit as follows:

- Create a project *addersubtractor*.
- Include a file *addersubtractor.v*, which corresponds to Figure 2, in the project. For convenience, this file is provided in the directory *DE2_tutorials\design_files*, which is included on the CD-ROM that accompanies the DE2 board and can also be found on Altera's DE2 web pages.
- Choose the Cyclone II EP2C35F672C6 device, which is the FPGA chip on Altera's DE2 board.
- Compile the design.

```

// Top-level module
module addersubtractor (A, B, Clock, Reset, Sel, AddSub, Z, Overflow);
  parameter n = 16;
  input [n-1:0] A, B;
  input Clock, Reset, Sel, AddSub;
  output [n-1:0] Z;
  output Overflow;
  reg SelR, AddSubR, Overflow;
  reg [n-1:0] Areg, Breg, Zreg;
  wire [n-1:0] G, H, M, Z;
  wire carryout, over_flow;

// Define combinational logic circuit
  assign H = Breg ^ {n{AddSubR}};
  mux2to1 multiplexer (Areg, Z, SelR, G);
  defparam multiplexer.k = n;
  adder nbit_adder (AddSubR, G, H, M, carryout);
  defparam nbit_adder.k = n;
  assign over_flow = carryout ^ G[n-1] ^ H[n-1] ^ M[n-1];
  assign Z = Zreg;

// Define flip-flops and registers
  always @(posedge Reset or posedge Clock)
    if (Reset == 1)
      begin
        Areg <= 0; Breg <= 0; Zreg <= 0;
        SelR <= 0; AddSubR <= 0; Overflow <= 0;
      end
    else
      begin
        Areg <= A; Breg <= B; Zreg <= M;
        SelR <= Sel; AddSubR <= AddSub; Overflow <= over_flow;
      end
    endmodule

// k-bit 2-to-1 multiplexer
module mux2to1 (V, W, Selm, F);
  parameter k = 8;
  input [k-1:0] V, W;
  input Selm;
  output [k-1:0] F;
  reg [k-1:0] F;

  always @(V or W or Selm)
    if (Selm == 0) F = V;
    else F = W;
endmodule

... continued in Part b

```

Figure 2. Verilog code for the circuit in Figure 1 (Part a).

```

// k-bit adder
module adderk (carryin, X, Y, S, carryout);
    parameter k = 8;
    input [k-1:0] X, Y;
    input carryin;
    output [k-1:0] S;
    output carryout;
    reg [k-1:0] S;
    reg carryout;

    always @(X or Y or carryin)
        {carryout, S} = X + Y + carryin;
endmodule

```

Figure 2. Verilog code for the circuit in Figure 1 (Part b).

2 Timing Analyzer Report

Successful compilation of our circuit generates the Compilation Report in Figure 3. This report provides a lot of useful information. It shows the number of logic elements, flip-flops (called registers), and pins needed to implement the circuit. It gives detailed information produced by the Synthesis and Fitter modules. It also indicates the speed of the implemented circuit. A good measure of the speed is the maximum frequency at which the circuit can be clocked, referred to as *f_{max}*. This measure depends on the longest delay along any path, called the *critical path*, between two registers clocked by the same clock. Quartus II software performs a timing analysis to determine the expected performance of the circuit. It evaluates several parameters, which are listed in the Timing Analyzer section of the Compilation Report. Click on the small + symbol next to Timing Analyzer to expand this section of the report, and then click on the Timing Analyzer item Summary which displays the table in Figure 4. The last entry in the table shows that the maximum frequency for our circuit implemented on the specified chip is 214.27 MHz. You may get a different value of *f_{max}*, dependent on the specific version of Quartus II software that you are using. To see the paths in the circuit that limit the *f_{max}*, click on the Timing Analyzer item Clock Setup: 'Clock' in Figure 4 to obtain the display in Figure 5. This table shows that the critical path begins at the flip-flop *AddSubR* and ends at the flip-flop *Overflow*.

Flow Summary	
Flow Status	Successful - Thu Sep 29 16:46:00 2005
Quartus II Version	5.0 Build 168 06/22/2005 SP 1 SJ Full Version
Revision Name	addersubtractor
Top-level Entity Name	addersubtractor
Family	Cyclone II
Device	EP2C35F672C6
Timing Models	Preliminary
Met timing requirements	Yes
Total logic elements	52 / 33,216 (< 1 %)
Total registers	51
Total pins	53 / 475 (11 %)
Total virtual pins	0
Total memory bits	0 / 483,840 (0 %)
Embedded Multiplier 9-bit elements	0 / 70 (0 %)
Total PLLs	0 / 4 (0 %)

Figure 3. The Compilation Report.

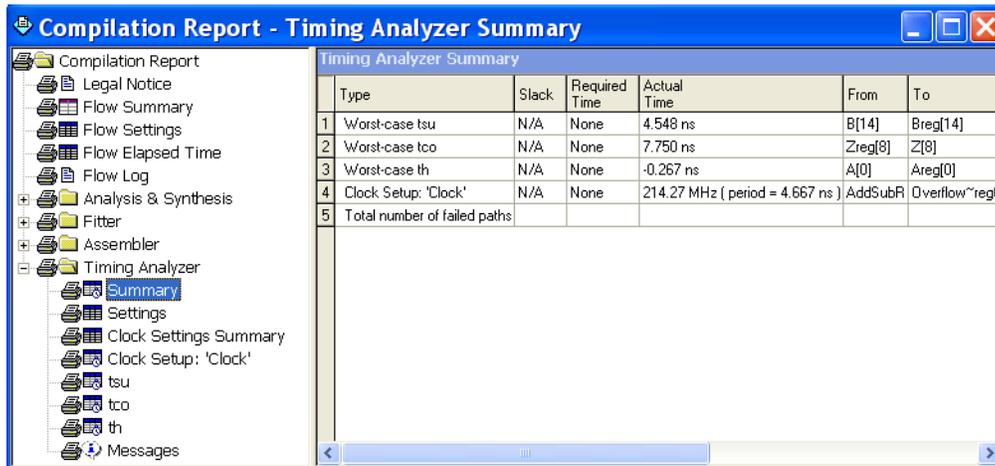


Figure 4. The Timing Analyzer Summary.

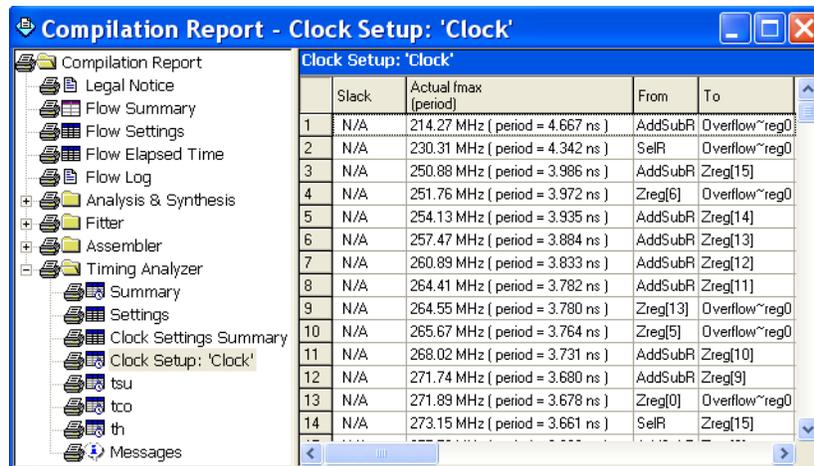


Figure 5. Critical paths.

The table in Figure 4 also shows other timing results. While f_{max} is a function of the longest propagation delay between two registers in the circuit, it does not indicate the delays with which output signals appear at the pins of the chip. The time elapsed from an active edge of the clock signal at the clock source until a corresponding output signal is produced (from a flip-flop) at an output pin is denoted as the t_{co} delay at that pin. In the worst case, the t_{co} in our circuit is 7.750 ns. Click on t_{co} in the Timing Analyzer section to view the table given in Figure 6. The first entry in the table shows that it takes 7.750 ns from when an active clock edge occurs until a signal propagates from bit 8 in register $Zreg$ to the output pin z_8 . The other two parameters given in Figure 4 are setup time, tsu , and hold time, th .

	Slack	Required tco	Actual tco	From	To	From Clock
1	N/A	None	7.750 ns	Zreg[8]	Z[8]	Clock
2	N/A	None	7.503 ns	Overflow~reg0	Overflow	Clock
3	N/A	None	7.456 ns	Zreg[12]	Z[12]	Clock
4	N/A	None	7.411 ns	Zreg[3]	Z[3]	Clock
5	N/A	None	7.328 ns	Zreg[2]	Z[2]	Clock
6	N/A	None	7.311 ns	Zreg[9]	Z[9]	Clock
7	N/A	None	7.196 ns	Zreg[6]	Z[6]	Clock
8	N/A	None	7.173 ns	Zreg[0]	Z[0]	Clock
9	N/A	None	7.093 ns	Zreg[11]	Z[11]	Clock
10	N/A	None	7.088 ns	Zreg[5]	Z[5]	Clock
11	N/A	None	7.072 ns	Zreg[10]	Z[10]	Clock
12	N/A	None	7.068 ns	Zreg[14]	Z[14]	Clock
13	N/A	None	7.046 ns	Zreg[13]	Z[13]	Clock
14	N/A	None	7.046 ns	Zreg[4]	Z[4]	Clock
15	N/A	None	6.801 ns	Zreg[1]	Z[1]	Clock
16	N/A	None	6.744 ns	Zreg[15]	Z[15]	Clock
17	N/A	None	6.547 ns	Zreg[7]	Z[7]	Clock

Figure 6. The *tco* delays.

3 Specifying Timing Constraints

So far we have compiled our Verilog code without indicating to the Quartus II software the required speed performance of the circuit. In the absence of such timing constraints the Quartus II software implements a designed circuit in a good but not necessarily the best way in order to keep the compilation time short. If the result does not meet the user's expectations, it is possible to specify certain timing constraints that should be met. For example, suppose that we want our example circuit to operate at a clock frequency of at least 250 MHz, rather than the 214.27 MHz as indicated by the value of *fmax* in Figure 4. To see if this can be achieved we can set the *fmax* constraint as follows:

1. Select Assignments > Timing Settings to reach the Timing Requirements & Options window in Figure 7. In this window it is possible to specify the requirements for a number of different parameters.
2. In the box Clock Settings specify that the required value of *fmax* is 250 MHz. Click OK.
3. Recompile the circuit.
4. Open the Timing Analyzer Summary to see that the new *fmax* is 263.02 MHz, as indicated in Figure 8. You may get a slightly different result depending on the version of the Quartus II software used.

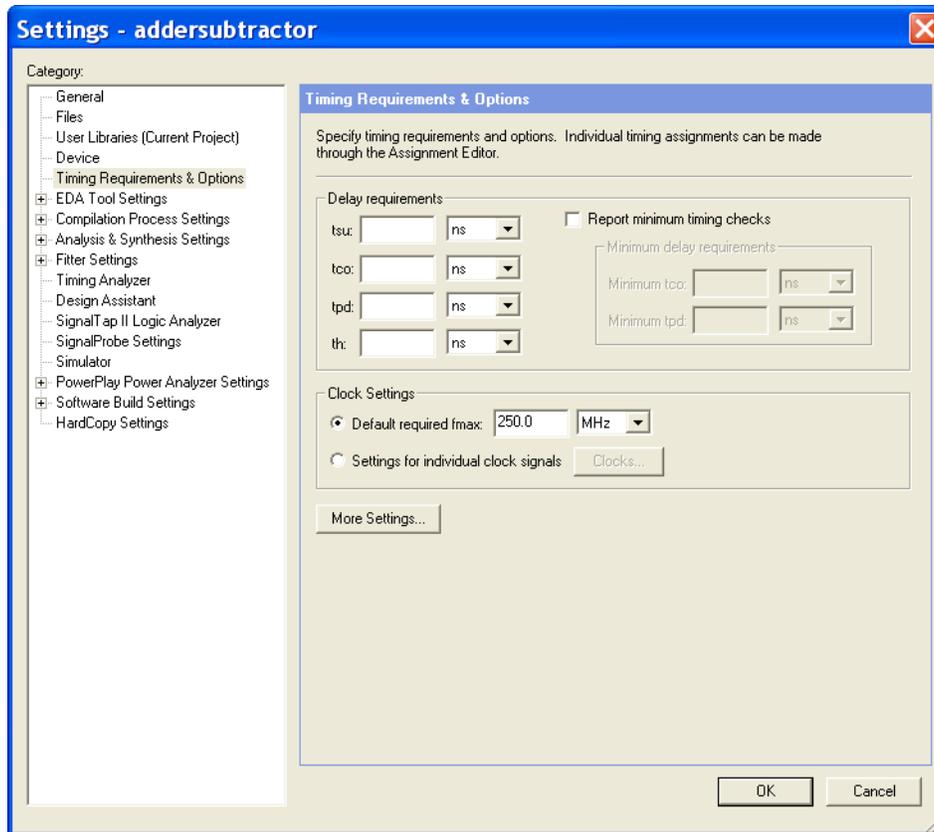


Figure 7. Specify the timing constraints in the Settings window.

Timing Analyzer Summary						
Type	Slack	Required Time	Actual Time	From	To	
1 Worst-case tsu	N/A	None	4.191 ns	A[15]	Areg[15]	
2 Worst-case tco	N/A	None	7.181 ns	Zreg[8]	Z[8]	
3 Worst-case th	N/A	None	-0.558 ns	Sel	SelR	
4 Clock Setup: 'Clock'	0.198 ns	250.00 MHz (period = 4.000 ns)	263.02 MHz (period = 3.802 ns)	AddSubR	Overflow~reg0	
5 Clock Hold: 'Clock'	1.175 ns	250.00 MHz (period = 4.000 ns)	N/A	Areg[0]	Zreg[0]	
6 Total number of failed paths						

Figure 8. New timing results.

If the specified constraint is too high, the Quartus II compiler will not be able to satisfy it. For example, set the *fmax* constraint to 300 MHz and recompile the circuit. Now, the Timing Analyzer Summary will show that this constraint cannot be met, as seen in Figure 9.

Type	Slack	Required Time	Actual Time	From	To
1 Worst-case tsu	N/A	None	4.191 ns	A[15]	Areg[15]
2 Worst-case tco	N/A	None	7.181 ns	Zreg[8]	Z[8]
3 Worst-case th	N/A	None	-0.558 ns	Sel	SelR
4 Clock Setup: 'Clock'	-0.469 ns	300.03 MHz (period = 3.333 ns)	263.02 MHz (period = 3.802 ns)	AddSubR	Overflow*reg0
5 Clock Hold: 'Clock'	1.175 ns	300.03 MHz (period = 3.333 ns)	N/A	Areg[0]	Zreg[0]
6 Total number of failed paths					

Figure 9. The timing constraint cannot be met.

The specified f_{max} of 300 MHz cannot be achieved because one or more paths in the circuit have long propagation delays. To locate the most critical path highlight the Clock Setup entry in the table by clicking on it. Then, right-click to get the pop-up menu shown in Figure 10. Select **Locate > Locate in RTL Viewer** which will cause the RTL Viewer to display the critical path as presented in Figure 11. Note that this path begins at flip-flop *AddSubR* and ends at the *Overflow* flip-flop.

Type	Slack	Required Time	Actual Time	From	To	Fro Clo
1 Worst-case tsu	N/A	None	4.191 ns	A[15]	Areg[15]	
2 Worst-case tco	N/A	None	7.181 ns	Zreg[8]	Z[8]	Clo
3 Worst-case th	N/A	None	-0.558 ns	Sel	SelR	
4 Clock Setup: 'Clock'	-0.469 ns	300.03 MHz (period = 3.333 ns)	263.02 MHz (period = 3.802 ns)	AddSubR	Overflow*reg0	Clo
5 Clock Hold: 'Clock'	1.175 ns	300.03 MHz (period = 3.333 ns)	N/A	Areg[0]	Zreg[0]	Clo
6 Total number of failed paths						

Figure 10. Locate the critical path.

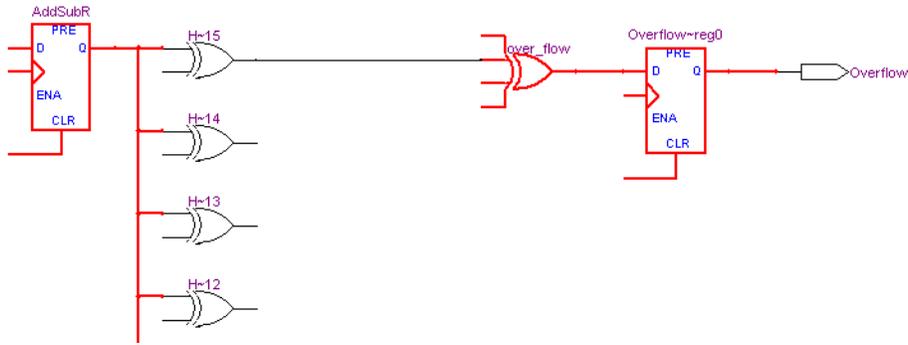


Figure 11. Path for which the timing constraint cannot be met.

It is likely that there are other paths that make it impossible to meet the specified constraint. To identify these paths choose **Clock Setup: 'Clock'** on the left side of the Compilation Report in Figure 9. As seen in Figure 12, there are 10 paths with propagation delays that are too long. Observe a column labeled *Slack*. The term *slack* is used to indicate the margin by which a timing requirement is met or not met. In the top row in Figure 12 we see that the timing delays along the path from the *AddSubR* flip-flop to the *Overflow* flip-flop are 0.469 ns longer than the maximum of 4 ns that is the period of the 250-MHz clock specified as the *fmax* constraint.

	Slack	Actual fmax (period)	From	To
1	-0.469 ns	253.02 MHz (period = 3.952 ns)	AddSubR	Overflow~reg0
2	-0.411 ns	267.09 MHz (period = 3.744 ns)	Zreg[5]	Overflow~reg0
3	-0.285 ns	276.40 MHz (period = 3.618 ns)	Zreg[0]	Overflow~reg0
4	-0.270 ns	277.55 MHz (period = 3.603 ns)	SelfR	Overflow~reg0
5	-0.247 ns	279.33 MHz (period = 3.580 ns)	Zreg[1]	Overflow~reg0
6	-0.191 ns	283.77 MHz (period = 3.524 ns)	Zreg[2]	Overflow~reg0
7	-0.152 ns	286.94 MHz (period = 3.485 ns)	Zreg[4]	Overflow~reg0
8	-0.146 ns	287.44 MHz (period = 3.479 ns)	Zreg[3]	Overflow~reg0
9	-0.063 ns	294.46 MHz (period = 3.396 ns)	Zreg[6]	Overflow~reg0
10	-0.049 ns	295.68 MHz (period = 3.382 ns)	Zreg[11]	Overflow~reg0
11	0.019 ns	301.75 MHz (period = 3.314 ns)	Breg[2]	Overflow~reg0
12	0.029 ns	302.66 MHz (period = 3.304 ns)	Zreg[7]	Overflow~reg0
13	0.118 ns	311.04 MHz (period = 3.215 ns)	Breg[4]	Overflow~reg0
14	0.123 ns	311.53 MHz (period = 3.210 ns)	Breg[0]	Overflow~reg0
15	0.163 ns	315.46 MHz (period = 3.170 ns)	Areg[0]	Overflow~reg0
16	0.174 ns	316.56 MHz (period = 3.159 ns)	Areg[11]	Overflow~reg0

Figure 12. The longest delay paths.

We have shown how to set the *fmax* constraint. The other constraints depicted in the window in Figure 7 can be set in the same way.

4 Timing Simulation

Timing simulation provides a graphical indication of the delays in the implemented circuit, as can be observed from the displayed waveforms. For a discussion of simulation see the tutorial *Quartus II Simulation with Verilog Designs*, which uses the same *addersubtractor* circuit as an example.

Copyright ©2005 Altera Corporation. All rights reserved. Altera, The Programmable Solutions Company, the stylized Altera logo, specific device designations, and all other words and logos that are identified as trademarks and/or service marks are, unless noted otherwise, the trademarks and service marks of Altera Corporation in the U.S. and other countries. All other product or service names are the property of their respective holders. Altera products are protected under numerous U.S. and foreign patents and pending applications, mask work rights, and copyrights. Altera warrants performance of its semiconductor products to current specifications in accordance with Altera's standard warranty, but reserves the right to make changes to any products and services at any time without notice. Altera assumes no responsibility or liability arising out of the application or use of any information, product, or service described herein except as expressly agreed to in writing by Altera Corporation. Altera customers are advised to obtain the latest version of device specifications before relying on any published information and before placing orders for products or services.

This document is being provided on an "as-is" basis and as an accommodation and therefore all warranties, representations or guarantees of any kind (whether express, implied or statutory) including, without limitation, warranties of merchantability, non-infringement, or fitness for a particular purpose, are specifically disclaimed.